


The objective of this homework is to test your understanding of the content of Module 3. Due date of the homework is: **Friday, February 5th, 2016.**

You have to upload a scanned version of your solutions on Blackboard. If you don't have a scanner around you, you can use Cam Scanner—a mobile app that scans images in a neat way, as if they're scanned through a copier. Here's the link for Cam Scanner: <https://www.camscanner.com/user/download>.

1. Linearize the following equation around  $x_0 = \pi/2$ :

$$y = f(x) = x^{1/3} + \cos(x).$$

2. For this circuit:

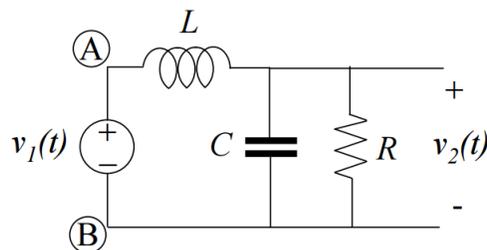

find,

- (a)  $\frac{V_2(s)}{V_1(s)}$  for any  $R, L, C$ .
- (b)  $v_2(t)$  if  $R = 1, L = 1, C = 1$ , and
  - i.  $v_1(t) = \delta(t)$ , or
  - ii.  $v_1(t) = 5$ .

This means that you have two different input voltage signals. Each signal will give a different output  $v_2(t)$  or  $V_2(s)$ .

After you analytically compute your answers, verify your solutions via MATLAB.